

Homework 4

Ian Eykamp

Oct 12, 2022

Implementation

I created python scripts to generate .sv files for arbitrarily-sized muxes and adders. They are both generated with recursive functions which compose the n -bit circuit from the smallest functional units, respectively the 2-bit mux and the 1-bit full adder.

The n -input mux is composed of $n-1$ 2-1 muxes arrayed in a logarithmic series as shown in Figure 1a. Assume n is a power of 2; otherwise, the inputs are padded with zeroes to make it a power of 2. This is composed recursively using the block shown in Figure 1b. Each recursive block contains a 2-1 mux which switches between two inputs, which are in turn generated by similar recursive blocks which each switch between half of the remaining inputs.

 


Figure 1.

I used the ripple carry implementation for the n -bit adder. The n -bit adder is composed of n 1-bit adders arranged in series, as shown in Figure 2a. This can also be composed recursively using the block shown in Figure 2b. Each recursive block appends a 1-bit adder onto the end of the previous recursive block.

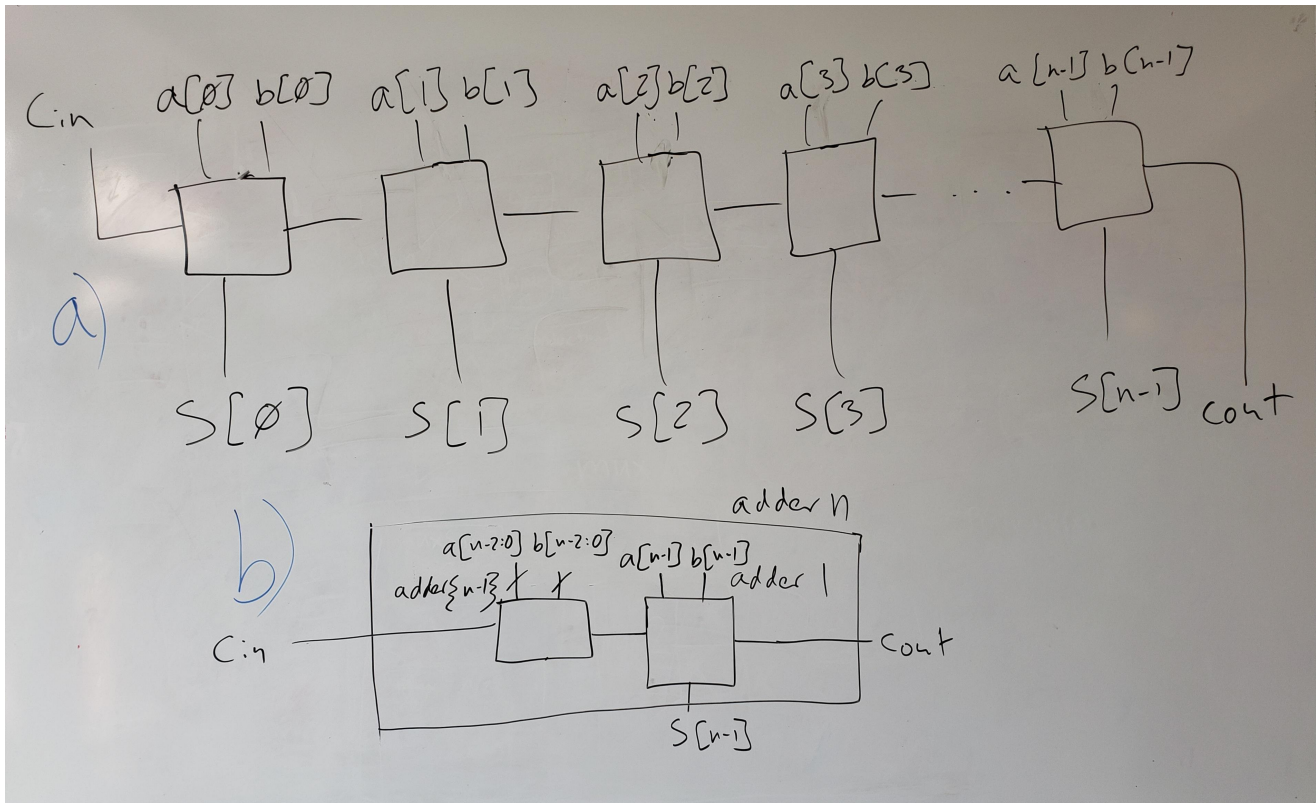


Figure 2.

Testing

It would be infeasible to test the 32-input mux and the 32-bit adder exhaustively, as this would require at least 2^{32} tests. My python scripts test the inputs exhaustively if and only if it would require fewer than 2^{10} runs; otherwise, they generate 2^{10} random input combinations to validate.

To run

Simply `make mux 32` and `make adder 32` will generate the required files and run the test scripts.

You should see a printout of no more than 2^{10} random test cases and the results of the test (success or failure).

You can also do this for any size of mux and any size of adder. Try `make mux 5` and `make adder 8`, for example.

It will also work for more than 32 inputs. Verilog doesn't like to generate more than 32-bit random numbers out of the box, so I concatenate digits to create arbitrarily-sized random bit strings for testing. Try `make mux 256` (it will take a few seconds to run).

Once you have done the `make` command, you can see the generated `.sv` files in the folders `generated_muxes` and `generated_adders`, respectively. There should be two `.sv` files for each size of mux / adder, for example `mux32.sv` and `test_mux32.sv`. One defines the `mux32` module and the other runs the test bench.